

TP Frequency mixer and amplifier

II. Measures

1) Characterization of local oscillator LO

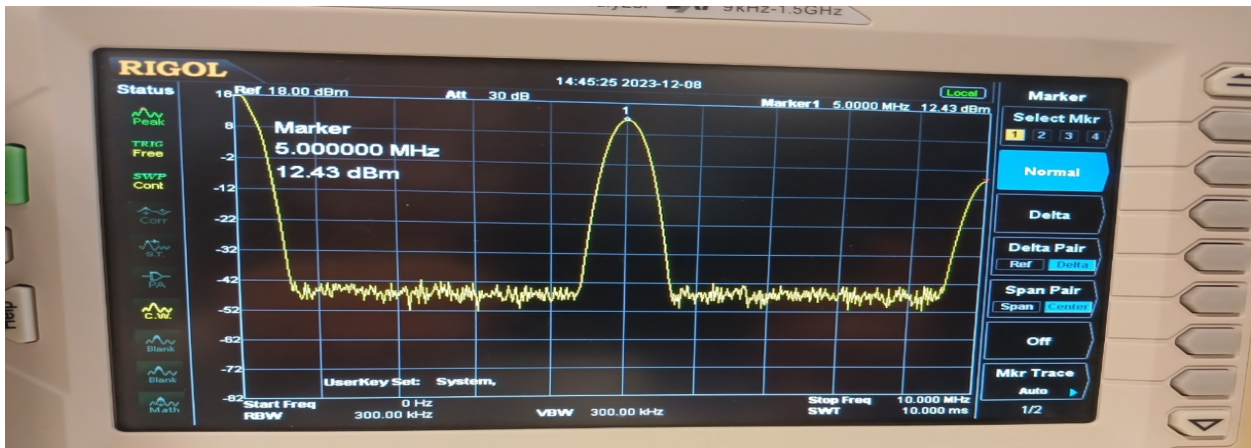


Figure.1.

We take a central frequency that presents high frequency at 5 MHz and then we obtain from Figure.1. $P=13$ dBm

2) Characterization of local oscillator LO

We add for the initial schematic a low pass filter for eliminate Image frequency so the intermodulation

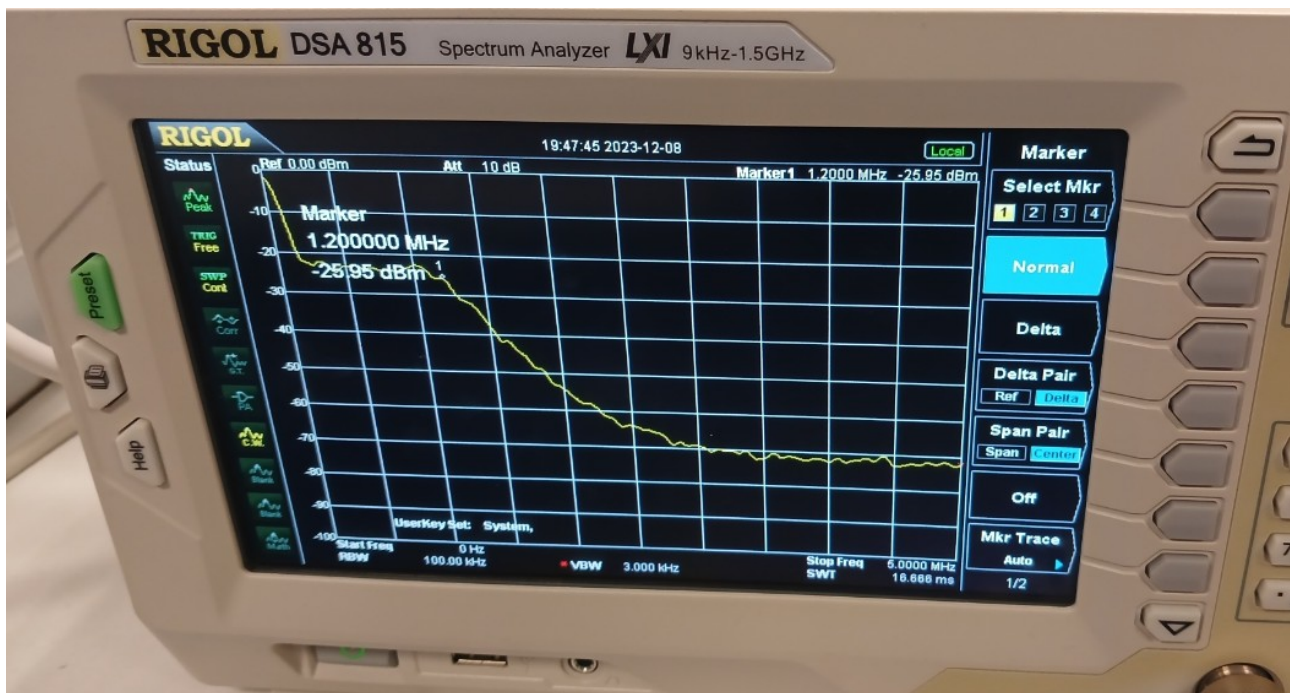


Figure.2.

We observe in Figure 2 low pass filter and before him we have some modulation due to parasitic resistor, after we put bandwidth for eliminate fluctuations; We remark flat band consequentely to the low pass filter, so he remove all the intermodulation.

We calculte cutoff frequency at -25,95dBm $F_0=1,2\text{MHz}$.

3) Characterization of Mixer

a)Identification of mixing products

$$RF=OL(+)-IF$$

$$RF=5\text{MHz}(+)-500\text{KHz}$$

1st case

we have RF high than IF

$$RF=5,5\text{MHz}$$

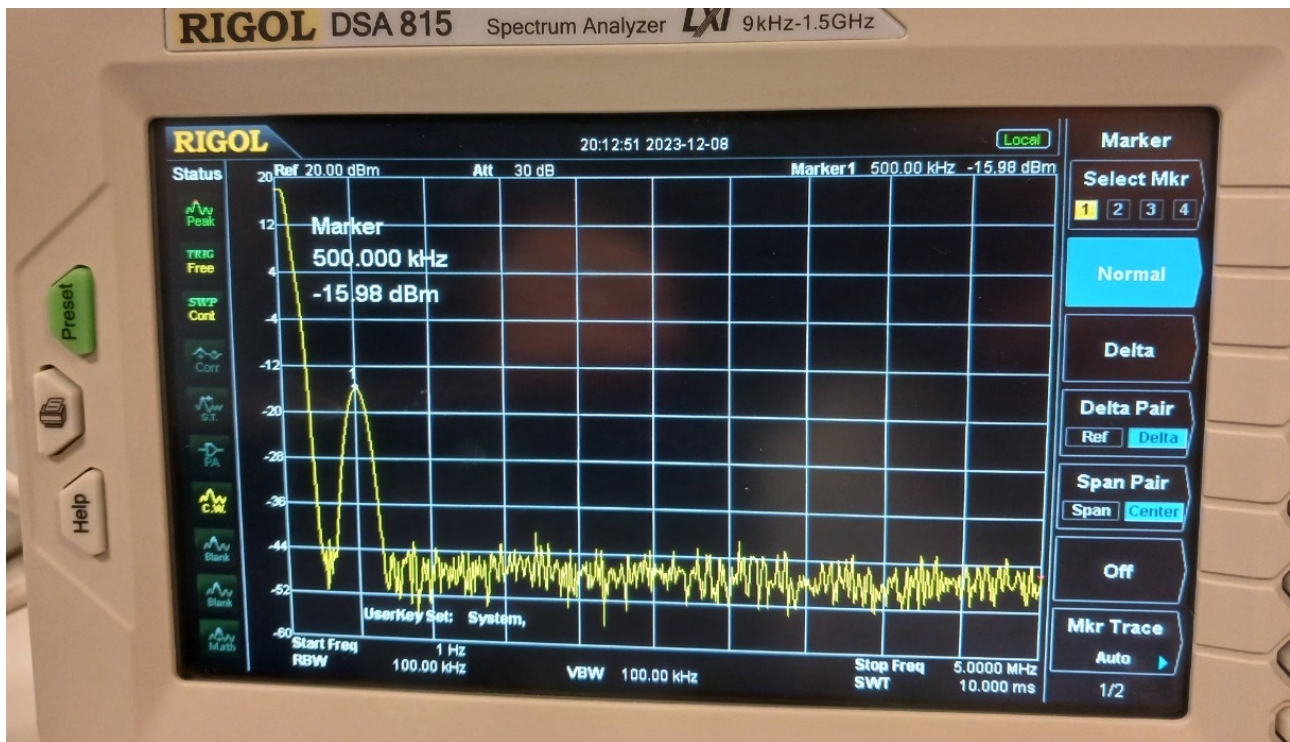


Figure.3.

from figure.3. we deduce this value
=-15

2nd case

RF=4,5MHz
=-14,8

We notice for the cases the values are the same

b) Conversion losses

1st case(RF=5,5MHz)

0dBm----- → -29,95dBm

5dBm----- → -35dBm

7dBm----- → -36,67dBm

2nd case(RF=4,5MHz)

0dBm----- → -29,95dBm

5dBm----- → -34,80dBm

7dBm----- → -36,70dBm

we notice that the both cases are the same

c) Isolation between ports

$$Is = OL_{OL} - OL_{IF}$$

$$Is = -44 - (-7)$$

$$Is = 37\text{dBm}$$

1st case(RF=5,5MHz)

$$Is(RF/IF) = P(\text{LO at LO}) - P(\text{LO at IF})$$

$$= 0 - (-40) = 40\text{dBm}$$

$$Is(\text{LO/IF}) = P(\text{LO at LO}) - P(\text{LO at IF})$$

$$= 7 - (-37) = 44\text{dBm}$$

2nd case(RF=4,5MHz)

$$Is(\text{LO/IF}) = P(\text{LO at LO}) - P(\text{LO at IF})$$

$$= 7 - (-44) = 51\text{dBm}$$

$$Is(RF/IF) = P(\text{RF at RF}) - P(\text{RF at IF})$$

$$= 0 - (-40) = 40\text{dBm}$$

$P(\text{IF at IF}) = -38\text{dBm}$

$P(\text{IF at LO}) = -50\text{dBm}$

$P(\text{LO at LO}) = 7\text{dBm}$